

# Chisel: Finite State Machines



Muhammad Tahir

Lecture 7

# Contents


- 1 Finite State Machines
- 2 Implementing State Machines
- 3 FSM Examples
- 4 The Arbiter


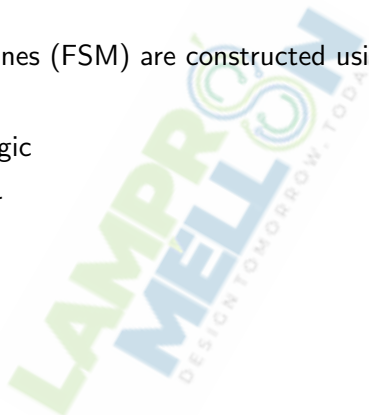
# Finite State Machines

Finite state machines (FSM) are constructed using three building blocks

- Next state logic
- State register
- Output logic



# Finite State Machines

Finite state machines (FSM) are constructed using three building blocks

- Next state logic
- State register
- Output logic

State machines can be of two types

- Mealy state machines
- Moore state machines

## Mealy State Machines

- Output of Mealy state machine depends on both state and input
- Can update the output faster?
- Is it synchronous or asynchronous?

 


Figure: Mealy type state machine.

# Moore State Machines

- Output of Moore state machine depends on state only
- Is it synchronous or asynchronous?

 


Figure: Moore type state machine.

# State Machine Construct

State machines can be constructed using Enum and switch construct

```
// The set of states
val s0 :: s1 :: s2 :: s3 :: s4 :: Nil = Enum(5)

// The state register
val state = RegInit(s0)

// Next state logic
switch (state) {
  is (s0){
    // state transition logic for s0
    // corresponds to outgoing arrows from s0
  }

  is (s1) {
  }

  ...

  is (s4) {
    // state transition logic for s4
  }
}
```

# Edge Detector

```
import chisel3._
import chisel3.util._

class Edge_FSM extends Module {
  val io = IO(new Bundle{
    val sin = Input(Bool())
    val edge = Output(Bool())
  })

  // Detect the edge
  io.edge = !io.sin & RegNext(io.sin)
}
```



## Edge Detector Cont'd

```
import chisel3._
import chisel3.util._

class Edge_FSM extends Module {
  val io = IO(new Bundle{
    val sin = Input(Bool())
    val edge = Output(Bool())
  })

  val zero :: one :: Nil = Enum(2) // The two states
  val state = RegInit(zero)        // The state register
  io.edge := false.B               // default value for output

  // Next state and output logic
  switch (state) {
    is(zero) {
      when(io.sin) {
        state := one
      }
    }

    is(one) {
      when(!io.sin) {
        state := zero
        io.edge := true.B
      }
    }
  }
}
```

## Up Down Counter

 


Figure: State transition diagram for up-down counter.

- What type of state machine is this?

## Up Down Counter

```
// up-down counter implementation

package LM_Chisel

import chisel3._
import chisel3.util._

class CounterUpDown(n: Int) extends Module {
  val io = IO(new Bundle {
    val data_in = Input(UInt(n.W))
    val out = Output(Bool())
  })

  val counter = RegInit(0.U(n.W))
  val max_count = RegInit(6.U(n.W))

  val init :: up :: down :: Nil = Enum(3) // Enumeration type
  val state = RegInit(init) // state = init
  val up_flag = (counter === max_count)
  val down_flag = (counter === 0.U)

  switch (state) {
    is (init) {
      state := up // on reset
    }

    is (up) {
      when (up_flag) {
        state := down
        // start count down immediately on up_flag
        counter := counter - 1.U
      }
    }
  }
}
```

## Up Down Counter Cont'd

```
    }.otherwise {  
      counter := counter + 1.U  
    }  
  }  
  
  is (down) {  
    when (down_flag) {  
      state := up  
      counter := counter + 1.U  
      max_count := io.data_in    // load the counter  
    }.otherwise {  
      counter := counter - 1.U  
    }  
  }  
}  
io.out := up_flag | down_flag  
}  
object CounterUpDown_generate extends App {  
  chisel3.Driver.execute(args, () => new CounterUpDown(8))  
}
```

# Up Down Counter Cont'd

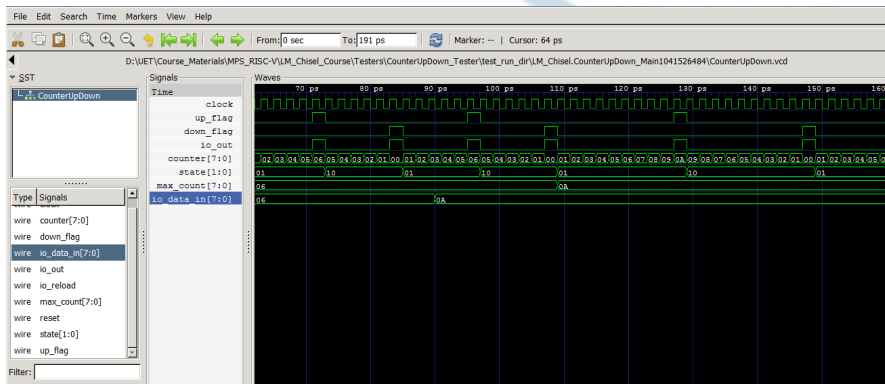


Figure: Up-down counter signal waveforms.

# UART Transmit

```
import chisel3._
import chisel3 . stage . ChiselStage
import chisel3.util._

case class UART_Params(
  dataBits:    Int = 8,
  stopBits:    Int = 2,
  divisorBits: Int = 5,
  oversample:  Int = 2,
  nSamples:    Int = 3,
  nTxEntries:  Int = 4,
  nRxEntries:  Int = 4) {
  def oversampleFactor = 1 << oversample
  require(divisorBits > oversample)
  require(oversampleFactor > nSamples)
}
```

## UART Transmit Cont'd

```
class UART_Tx(c: UART_Params) extends Module {  
  val io = IO(new Bundle {  
    val en      = Input(Bool())  
    val in      = Flipped(Decoupled(UInt((c.dataBits).W)))  
    val out     = Output(Bool())  
    val div     = Input(UInt((c.divisorBits).W))  
    val nstop   = Input(UInt((c.stopBits).W))  
  })  
  // pulses generated at baud rate using prescaler  
  val prescaler = RegInit(0.U((c.divisorBits).W))  
  val pulse     = (prescaler === 0.U)  
  private val n = c.dataBits + 1  
  
  val counter = RegInit(0.U((log2Floor(n + c.stopBits)+1).W))  
  val shifter = Reg(UInt(n.W))  
  val out     = RegInit(true.B)
```

## UART Transmit Cont'd

```
val busy      = (counter /= 0.U)
val state1    = io.en && !busy
val state2    = busy
io.in.ready   := state1

when(state1) {
  shifter := Cat(io.in.bits, false.B)
  counter := Mux1H(
    (0 until c.stopBits).map(i => (io.nstop == i.U) -> (n+i+2).U)
  )
}

when(state2) {
  prescaler := Mux(pulse, (io.div - 1.U), prescaler - 1.U)

  when(pulse) {
    counter := counter - (1.U)
    shifter := Cat(true.B, shifter >> 1)
    out := shifter(0)
  }
}

// Instantiation of the UART_Tx module for Verilog generator
object UART_Tx_generate extends App {
  val param = UART_Params()
  chisel3.Driver.execute(args, () => new UART_Tx(param))
}
```



# Arbiter

- A hardware module following data producer/consumer model
- Sequences  $n$  producers to 1 consumer
- Connects one of the producers, at a given time, to the consumer
- Connectivity follows a certain priority mechanism

## Chisel: Arbiter

```
val arb_priority = Module(new Arbiter(UInt(), 3))

// connect the inputs to different producers
arb_priority.io.in(0) <> producer0.io.out
arb_priority.io.in(1) <> producer1.io.out
arb_priority.io.in(2) <> producer2.io.out

// connect the output to consumer
consumer.io.in <> arb_priority.io.out
```

- An arbiter module with priority
- Lower indexed producer is given higher priority
- Uses `DecoupledIO` interface for input and output connectivity

## Chisel: RRArbiter

```
val arb_noPriority = Module(new RRArbiter(UInt(), 3))

// connect the inputs to different producers
arb_noPriority.io.in(0) <> producer0.io.out
arb_noPriority.io.in(1) <> producer1.io.out
arb_noPriority.io.in(2) <> producer2.io.out

// connect the output to consumer
consumer.io.in <> arb_noPriority.io.out
```

- An arbiter module with no or equal priority
- Each producer gets its turn in a round robin fashion

## Reading List I

- Consult [chisel3, 2020] for further details
- Read Chapter 8 of [Schoeberl, 2019]

# References



chisel3 (2020).

Chisel3 library reference.

<https://www.chisel-lang.org/api/latest/chisel3/util>.



Schoeberl, M. (2019).

*Digital Design with Chisel.*

Kindle Direct Publishing.