Chisel: Sequential Circuits



Muhammad Tahir*

Lecture 6

Contents

- Sequential Circuits
- 2 The Register and Its Variants
- 3 Counters and Timers
- 4 Register File





Sequential Circuits

- Sequential circuits are used to implement states and state elements
- State machines and memories can be constructed from sequential circuits



Reg

- Registers are fundamental elements to build sequential circuits
- Register implementation using single or multiple D-type flip-flops
- Chisel provides object Reg for constructing hardware registers

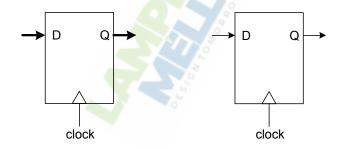


Figure: Single- or multi-bit register.



RegNext


- Width can be inferred or specified
- Can be used to get one cycle delayed version of the signal

```
// following uses of Reg and RegNext are valid
val reg1 = Reg(UInt(8.W))
val reg2 = RegNext(reg1)
                         // width is inferred from reg1
val reg3 = RegNext(3.U(8.W))
                              // width is specified
// following uses are invalid
val reg4 = Reg(3.U(8.W))
val reg5 = RegNext(UInt(8.W))
```



RegInit

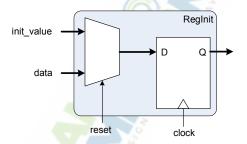- Register with initialized value
- Initialization occurs on reset



```
// following uses of RegInit are valid
val reg1 = RegInit(24.U(8.W))
val reg2 = Reg(UInt(8.W))
val reg3 = RegInit(reg2)
// following uses are invalid
val reg1 = RegInit(0.U(UInt(8.W)))
val reg2 = RegInit(UInt(8.W))
```



RegEnable


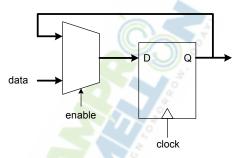


Figure: Register with enable input.
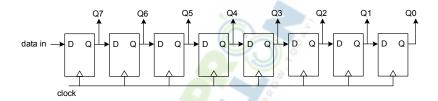
```
val regWithEnable = RegEnable(nextVal, ena)
```



Shift Register: Serial In Parallel Out



```
shift register (serial in and parallel out)
val shiftReg = RegInit(0.U(n.W))
   shift register implementation
shiftReg := Cat(data_in , shiftReg (n-1, 1))
val Q = shiftReg
```




Shift Register: Implementation

```
// shift register example
import chisel3._
class shift_reg(val init: Int = 1) extends Module {
    val io = IO(new Bundle{
        val in = Input(Bool())
        val out = Output(UInt(4.W))
    })
    // register initialization
    val state = RegInit(init.U(4.W))
    // serial data in at LSB
    val nextState = (state << 1) | io.in</pre>
    state := nextState
    io.out := state
println((new chisel3.stage.ChiselStage).emitVerilog(new
    shift_reg))
```



Counter

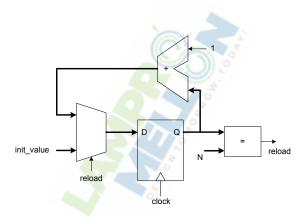



Counter Cont'd

Counters and Timers 00000

```
// Optimized counter example
import chisel3._
import chisel3.util._
class counter(val max: Int, val min: Int = 0) extends Module
   val io = IO(new Bundle{
        val out = Output(UInt(log2Ceil(max).W))
   })
   val counter = RegInit(min.U(log2Ceil(max).W))
   // If the max count is of power 2 and the min value = 0,
   // then we can skip the comparator and the Mux
   val count buffer = if (isPow2(max) && (min == 0))
      counter + 1.U
    else Mux(counter === max.U, min.U, counter + 1.U)
    counter := count buffer
    io.out := counter
println((new chisel3.stage.ChiselStage).emitVerilog(new
    counter(32)))
```





PWM Generation

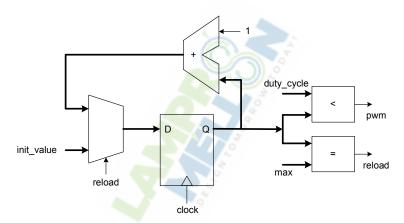



Figure: Block diagram for PWM generation.



PWM Generation Cont'd

```
// PWM example
import chisel3._
import chisel3.util._
class PWM(val max: Int = 2, val duty_cycle: Int = 1) extends
    Module {
   val io = IO(new Bundle {
        val out = Output(Bool())
   })
   val counter = RegInit(0.U(log2Ceil(max).W))
    counter := Mux(counter === max.U, 0.U, counter+1.U)
   io.out := duty_cycle.U > counter
println((new chisel3.stage.ChiselStage).emitVerilog(new PWM
    (15)))
```



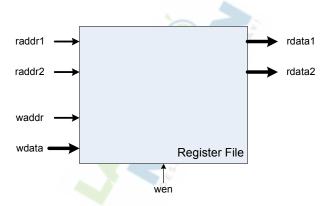



Implementing Register File

```
import chisel3._
class RegFileIO extends Bundle with Config {
    val raddr1 = Input(UInt(5.W))
    val raddr2 = Input(UInt(5.W))
    val rdata1 = Output(UInt(XLEN.W))
    val rdata2 = Output(UInt(XLEN.W))
    val wen = Input(Bool())
    val waddr = Input(UInt(5.W))
    val wdata = Input(UInt(XLEN.W))
class RegFile extends Module with Config {
    val io = IO(new RegFileIO)
    val regs = Reg(Vec(REGFILE_LEN, UInt(XLEN.W)))
    io.rdata1 := Mux((io.raddr1.orR), regs(io.raddr1), 0.U)
    io.rdata2 := Mux((io.raddr2.orR), regs(io.raddr2), 0.U)
    when (io.wen & io.waddr.orR) {
         regs(io.waddr) := io.wdata
    }
```



Queues

- Queue interface using Decoupled
- Implements gueue with 16 elements

```
import chisel3._
import chisel3.util._
class User_Queue extends Module {
   val io = IO(new Bundle {
       //valid is Input, ready is Output, bits is Input
        val in = Flipped(Decoupled(UInt(8.W)))
       //valid is Output, ready is Input , bits is Output
        val out = Decoupled(UInt(8.W))
   })
   // 16 element queue
   val queue = Module(new Queue(UInt(), 16))
    queue.io.enq <> io.in
    io.out <> queue.io.deq
println(chisel3.Driver.emitVerilog(new User_Queue))
```



BlackBox

- Integration of existing Verilog IP is an essential requirement
- Chisel solution to this problem is BlackBox
- BlackBox is instantiated in the generated Verilog
- No implicit clock or reset in BlackBox, explicit connectivity required for this purpose



Adder implementation using BlackBox

```
class BlackBoxAdder extends BlackBox with
   HasBlackBoxResource {
   val io = IO(new Bundle() {
        val in1 = Input(UInt(32.W))
        val in2 = Input(UInt(32.W))
        val out = Output(UInt(33.W))
   })
    setResource ("/Adder.v")
```



BlackBox Cont'd

Adder implementation using BlackBox with inline Verilog

```
class BlackBoxAdder extends BlackBox with HasBlackBoxInline
   val io = IO(new Bundle() {
        val in1 = Input(UInt(32.W))
        val in2 = Input(UInt(32.W))
        val out = Output(UInt(33.W))
   })
    setInline ("BlackBoxAdder.v",
    s " " "
     module BlackBoxAdder(
      input [32:0] in1,
      input [32:0] in2,
     output [33:0] out
     always @* begin
     out <= ((in1) + (in2));
     end
    endmodule
    """.stripMargin)
```



- Read the relevant sections from Chapter 6 of [Schoeberl, 2019]
- Consult [chisel3, 2020] for further details





chisel3 (2020).

Chisel3 library reference.

https://www.chisel-lang.org.



Schoeberl, M. (2019).

Digital Design with Chisel.

Kindle Direct Publishing.

