

Chisel: Control Flow & Combinational Circuits



Muhammad Tahir*

Lecture 3

Contents

① Conditional Constructs

Chisel when construct

Chisel switch construct

② The ALU Module


③ ALU Implementation

④ Valid and ReadyValid Interfaces



Conditional Constructs

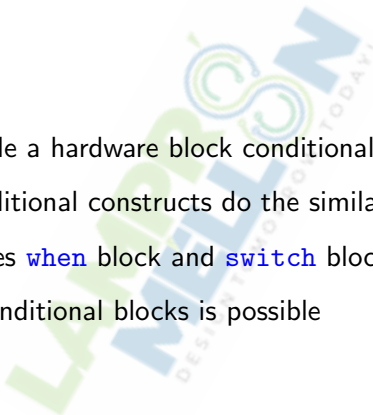- Used to enable a hardware block conditionally
- Multiple conditional constructs do the similar job
- Chisel provides `when` block and `switch` block
- Nesting of conditional blocks is possible



Encoder Decoder Block Diagram

Illustration of **when** and **switch** using encoder and decoder modules

 


Figure: Encoder (4 to 2) and decoder (2 to 4).

Chisel: when Syntax

```
when(/* condition for when */){  
    /* do this if the condition for when is true */  
}  
.elsewhen(/* condition for elsewhen */){  
    /* do this if the when is false and  
    condition for .elsewhen is true. */  
}  
.otherwise{  
    /* do this as a default condition, .otherwise  
    do not require a condition as it is the default  
    when no previous condition is met. */  
}
```

Chisel: when

Implementing 4 to 2 Encoder with when

```
class EncoderIO extends Bundle {  
  val in  = Input(UInt(4.W))  
  val out = Output(UInt(2.W))  
}  
  
class Encoder4to2 extends Module {  
  val io = IO(new EncoderIO)  
  
  when (io.in === "b0001".U) {  
    io.out := "b00".U  
  } .elsewhen(io.in === "b0010".U) {  
    io.out := "b01".U  
  } .elsewhen(io.in === "b0100".U) {  
    io.out := "b10".U  
  } .otherwise {  
    io.out := "b11".U  
  }  
}
```



Chisel: switch Syntax

```
switch (state) {  
  is(state1){  
    // logic implementation which runs when state ==  
    state1  
  }  
  is(state2){  
    // logic implementation which runs when state ==  
    state1  
  }  
  // what about the default state  
}
```



Chisel: switch

```
class DecoderIO extends Bundle {  
  val in  = Input(UInt(2.W))  
  val out = Output(UInt(4.W))  
}  
  
class Decoder2to4 extends Module {  
  val io = IO(new DecoderIO)  
  io.out := 0.U  
  switch (io.in) {  
    is ("b00".U) {  
      io.out := "b0001".U  
    }  
    is ("b01".U) {  
      io.out := "b0010".U  
    }  
    is ("b10".U) {  
      io.out := "b0100".U  
    }  
    is ("b11".U) {  
      io.out := "b1000".U  
    }  
  }  
}
```


ALU Module

 


Figure: ALU block diagram representation.

ALU Operations

Define ALU operations using Scala **object**

```
object ALUOP {  
  // ALU Operations, may expand/modify in future  
  val ALU_ADD      = 0.U(4.W)  
  val ALU_SUB      = 1.U(4.W)  
  val ALU_AND      = 2.U(4.W)  
  val ALU_OR       = 3.U(4.W)  
  val ALU_XOR      = 4.U(4.W)  
  val ALU_SLT      = 5.U(4.W)  
  val ALU_SLL      = 6.U(4.W)  
  val ALU_SLTU     = 7.U(4.W)  
  val ALU_SRL      = 8.U(4.W)  
  val ALU_SRA      = 9.U(4.W)  
  val ALU_COPY_A   = 10.U(4.W)  
  val ALU_COPY_B   = 11.U(4.W)  
  val ALU_XXX      = 15.U(4.W)  
}
```

Listing 1: ALU operations.

ALU Implementation: MuxLookup

```
import ALUOP._

trait Config {
  // global config parameters
  val WLEN      = 32
  val XLEN      = 32
  val ALUOP_SIG_LEN = 4 // control signal's width
}

class AluIO extends Bundle with Config {
  val in_A      = Input(UInt(WLEN.W))
  val in_B      = Input(UInt(WLEN.W))
  val alu_Op     = Input(UInt(ALUOP_SIG_LEN.W))
  val out       = Output(UInt(WLEN.W))
}
```

ALU Implementation: MuxLookup Cont'd

```
class Alu_Lookup extends Module with Config {
  val io = IO(new AluIO)

  val shamt = io.in_B(4,0).asUInt

  io.out := MuxLookup(io.alu_Op, io.in_B, Seq(
    ALU_ADD   -> (io.in_A + io.in_B),
    ALU_SUB   -> (io.in_A - io.in_B),
    ALU_SRA   -> (io.in_A .asSInt >> shamt).asUInt,
    ALU_SRL   -> (io.in_A >> shamt),
    ALU_SLL   -> (io.in_A << shamt),
    ALU_SLT   -> (io.in_A .asSInt < io.in_B.asSInt),
    ALU_SLTU  -> (io.in_A < io.in_B),
    ALU_AND   -> (io.in_A & io.in_B),
    ALU_OR    -> (io.in_A | io.in_B),
    ALU_XOR   -> (io.in_A ^ io.in_B),
    ALU_COPY_A -> io.in_A ))
}
```

ALU Implementation: Optimized

```
class ALU extends Module with Config {
  val io = IO(new AluIO)

  val sum      = io.in_A + Mux(io.alu_Op(0), -io.in_B, io.in_B)
  val cmp      = Mux(io.in_A (XLEN-1) === io.in_B(XLEN-1), sum(XLEN-1),
                    Mux(io.alu_Op(1), io.in_B(XLEN-1), io.in_A(XLEN-1)))
  val shamt    = io.in_B(4,0).asUInt
  val shin     = Mux(io.alu_Op(3), io.in_A, Reverse(io.in_A))
  val shiftr   = (Cat(io.alu_Op(0) && shin(XLEN-1), shin).asSInt >>
                  shamt) (XLEN-1, 0)

  val shiftl   = Reverse(shiftr)

  val out =
    Mux(io.alu_Op === ALU_ADD.U || io.alu_Op === ALU_SUB.U, sum,
    Mux(io.alu_Op === ALU_SLT.U || io.alu_Op === ALU_SLTU.U, cmp,
    Mux(io.alu_Op === ALU_SRA.U || io.alu_Op === ALU_SRL.U, shiftr,
    Mux(io.alu_Op === ALU_SLL.U, shiftl,
    Mux(io.alu_Op === ALU_AND.U, (io.in_A & io.in_B),
    Mux(io.alu_Op === ALU_OR.U, (io.in_A | io.in_B),
    Mux(io.alu_Op === ALU_XOR.U, (io.in_A ^ io.in_B),
    Mux(io.alu_Op === ALU_COPY_A.U, io.in_A,
    Mux(io.alu_Op === ALU_COPY_B.U, io.in_B, 0.U)))))))))

  io.out := out
}
```

Comparing ALU Implementations

Table: ALU resource usage comparison for different implementations.

Parameter	MuxLookUp Based	Optimized
Slice LUTs as Logic	440	230
F7 Muxes	28	0
Bonded IOB Pads	132	132
Primitives, LUT2, LUT3, LUT4	52, 76, 75	2, 79, 3
Primitives, LUT5, LUT6	45, 252	53, 126
Primitives, CARRY4	32	8

Valid Interface

- A Bundle which adds valid bit to the data
- When valid data is put on data lines (bits) by the producer, it asserts valid bit
- Producer does not wait for the consumer

 


Figure: Valid signal for producer and consumer model.

Valid Interface Cont'd

- **object** **Valid** acts as factory to generate **Valid** interfaces
- Wraps the data by calling the companion object of **class** **Valid**

```
// data bits without valid signal
class DataWithoutValid extends Bundle {
  val data_bits = Output(UInt(8.W))
}
```

```
// data bits with valid signal
val DataWithValid = Valid(new
  DataWithoutValid)
```



```
// data bits without valid signal
class DataWithoutValid extends Bundle {
  val data_bits = Output(UInt(8.W))
}

class DataWithValid extends Bundle {
  val valid = Output(Bool())
  val data = Output(new
    DataWithoutValid)
}
```


Ready Valid Interface

- A bundle providing *valid* and *ready* signals for handshaking
- Producer uses the interface as is
- The consumer uses flipped interface

 


Figure: Ready valid signaling for producer and consumer model.

Ready Valid Interface

- *valid* indicates that the producer has put valid data on data lines/bits
- *ready* indicates that the consumer is ready to accept the data this cycle
- No signaling requirements are imposed on ready and valid

```
class ReadyValidIO[T <: Data](gen: T) extends Bundle {  
  val ready = Input(Bool())  
  val valid = Output(Bool())  
  val bits = Output(gen)  
}
```

DecoupledIO and Decoupled

- DecoupledIO is a subclass of ReadyValidIO signaling

```
// DecoupledIO class definition  
class DecoupledIO[+T <: Data] extends ReadyValidIO[T]
```

- The **object** Decoupled wraps/adds a ready-valid handshaking protocol to the data bundle
- The **apply** method of Decoupled adds the handshaking protocol using the DecoupledIO

Reading List

- Read the relevant sections from Chapters 2 and 4 of [Schoeberl, 2019]
- Also consult the [chisel3, 2020] for further details
- For type parameters and associated variance read Sections 19.3 to 19.6 of [Odersky et al., 2016]

References



chisel3 (2020).

Chisel3 library reference.

<https://www.chisel-lang.org>.



Odersky, M., Spoon, L., and Venners, B. (2016).

Programming in Scala.

Artima Incorporation.



Schoeberl, M. (2019).

Digital Design with Chisel.

Kindle Direct Publishing.