

Chisel: Combinational Circuits



Muhammad Tahir

Lecture 2

Contents

① Chisel: Supported Operations

② The Multiplexer

③ Mux Utilities

PriorityMux and Mux1H

MuxCase

④ Bundles and Vec

Supported Operations

- All supported operations are implemented as Combinational Circuits
- Can be performed with single or bundle of wires (with few exceptions)
- Operator precedence is determined by the evaluation order of the circuit (and follows Scala operator precedence)

Chisel Hardware Operations

Table: Different groups of hardware operations.

Operator Symbol	Description	Operand Type
&& !	AND, OR, NOT (logical)	Bool
& ~ ^	AND, OR, NOT, XOR (bitwise)	UInt, SInt, Bool
<< >>	shift left, shift right (sign extend for SInt)	UInt, SInt
+ -	addition, subtraction	UInt, SInt
* / %	multiplication, division, modulus	UInt, SInt
=== = / =	equal, not equal (returns Bool)	UInt, SInt
> >= < <=	different comparisons (returns Bool)	UInt, SInt

Chisel Hardware Operations Cont'd

More on arithmetic operations

```
// Arithmetic operations

// Addition without width expansion
val sum = x + y // OR
val sum = x +%y

// Addition with width expansion
val sum = x +&y

// Subtraction without width expansion
val sum = x - y // OR
val sum = x -%y

// Subtraction with width expansion
val sum = x -&y
```

Chisel Hardware Operations Cont'd

Bitfield manipulations and reductions

```
// Bitfield manipulations
val xMSB = x(31)           // when x is 32-bit
val yLowByte = y(7, 0)    // y is atleast 8-bit

// concatenates bitfields with first operand on left
val address = Cat(highByte, lowByte)

// replicate a string multiple times
val duplicate = Fill(2, "b1010".U) // "b10101010".U

// Bitfield reductions
val data = "b00111010".U
val allOnes = data.andR           // performs AND reduction
val anyOne = data.orR             // performs OR reduction
val parityCheck = data.xorR       // performs XOR reduction
```

Width Inference for Hardware Operations

Rules to infer width at the output of hardware block

Table: Bit Width Inference*.

Operation	Bit Width
$\text{out} = \text{in1} + \text{in2}$	$W(\text{out}) = \max\{W(\text{in1}), W(\text{in2})\}$
$\text{out} = \text{in1} +\& \text{in2}$	$W(\text{out}) = \max\{W(\text{in1}), W(\text{in2})\} + 1$
$\text{out} = \text{in1} \& \text{in2}$	$W(\text{out}) = \max\{W(\text{in1}), W(\text{in2})\}$
$\text{out} = \text{in1} * \text{in2}$	$W(\text{out}) = W(\text{in1}) + W(\text{in2})$
$\text{out} = \text{in1} \ll \text{shift}$	$W(\text{out}) = W(\text{in1}) + \max(\text{shift})$
$\text{out} = \text{in1} \gg \text{shift}$	$W(\text{out}) = W(\text{in1}) - \min(\text{shift})$
$\text{out} = \text{Cat}(\text{in1}, \text{in2})$	$W(\text{out}) = W(\text{in1}) + W(\text{in2})$

* where $W(x)$ is the bit width of signal or wire x .

Mux Block

One of the most widely used hardware blocks

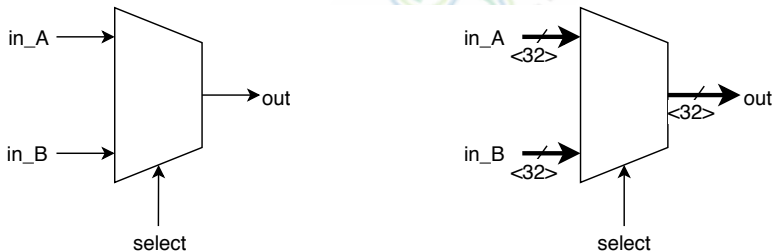


Figure: A simple 2 to 1 Mux.

Mux Block Cont'd

Mux 2 to 1 (scalar (Bool) inputs)

```
import chisel3._

// Mux IO interface class
class Mux_2to1_IO extends Bundle {
  val in_A    = Input(Bool())
  val in_B    = Input(Bool())
  val select  = Input(Bool())
  val out     = Output(Bool())
}

// 2 to 1 Mux implementation
class Mux_2to1 extends Module {
  val io = IO(new Mux_2to1_IO)

  // update the output
  io.out := io.in_A & io.select | io.
    in_B & (~io.select)
}

println((new chisel3.stage.ChiselStage).
  emitVerilog(new Mux_2to1()))
```

Mux 2 to 1 (vector inputs)

```
import chisel3._

// Mux IO interface class
class Mux_2to1_IO extends Bundle {
  val in_A    = Input(UInt(32.W))
  val in_B    = Input(UInt(32.W))
  val select  = Input(Bool())
  val out     = Output(UInt())
}


// 2 to 1 Mux implementation
class Mux_2to1 extends Module {
  val io = IO(new Mux_2to1_IO)

  // update the output
  io.out := Mux(io.select, io.in_A, io.
    in_B)
}

println((new chisel3.stage.ChiselStage).
  emitVerilog(new Mux_2to1()))
```

Mux Block: Mux4to1

Mux 4 to 1 with 2 selection lines

 

Mux Block: Mux4to1

Mux 4 to 1 implementation

```
// Mux4to1 example
import chisel3._

class IO_Interface extends Bundle {
  val in  = Input(UInt(4.W))
  val s1  = Input(Bool())
  val s2  = Input(Bool())
  val out = Output(Bool())    // UInt(1.W))
}


class Mux_4to1 extends Module {
  val io = IO(new IO_Interface)

  io.out := Mux(io.s2, Mux(io.s1, io.in(3), io.in(2)),
    Mux(io.s1, io.in(1), io.in(0)))
}

println((new chisel3.stage.ChiselStage).emitVerilog(new
  Mux_4to1()))
```

Mux Tree: Mux4to1

 - Mux 4 to 1 with 3 selection lines
- Available as PriorityMux from utilities



Mux Tree: Mux4to1

Mux 4 to 1 using priority implementation

```
// Mux with input priority
import chisel3._

class IO_Interface extends Bundle {
  val in  = Input(UInt(4.W))
  val s1  = Input(Bool())
  val s2  = Input(Bool())
  val s3  = Input(Bool())
  val out = Output(Bool())    // UInt(1.W))
}


class Mux_Tree extends Module {
  val io = IO(new IO_Interface)

  io.out := Mux(io.s3, io.in(3), Mux(io.s2, io.in(2),
  Mux(io.s1, io.in(1), io.in(0))))
}

println((new chisel3.stage.ChiselStage).emitVerilog(new
  Mux_Tree()))
```

Mux1H

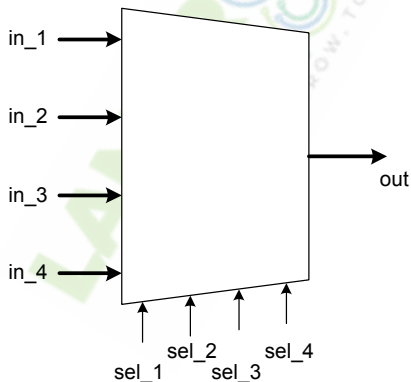- 4 to 1 Mux with 4 selection lines
- Available as Mux1H from utilities



MuxCase

```
// 4 to 1 mux using MuxCase
import chisel3._
import chisel3.util._

class MuxCase_Example extends Module {
  val io = IO(new Bundle{
    val in0 = Input(Bool())
    val in1 = Input(Bool())
    val in2 = Input(Bool())
    val in3 = Input(Bool())
    val sel = Input(UInt(2.W))
    val out = Output(Bool())
  })

  io.out := MuxCase(false.B, Array(
    (io.sel === 0.U) -> io.in0,
    (io.sel === 1.U) -> io.in1,
    (io.sel === 2.U) -> io.in2,
    (io.sel === 3.U) -> io.in3
  ))
}

println((new chisel3.stage.ChiselStage).emitVerilog(new MuxCase_Example ()))
```

MuxLookup

MuxLookup is similar to MuxCase with slightly different syntax

```
// MuxLookup example
val raw_data = io.dmem.rdata
val load_data = MuxLookup(ld_type, 0.U,
                          Seq(LD_LW -> raw_data.zext,
                              LD_LH  -> raw_data(15, 0).asSInt,
                              LD_LB  -> raw_data(7, 0).asSInt,
                              LD_LHU -> raw_data(15, 0).zext,
                              LD_LBU -> raw_data(7, 0).zext))
```


Bundles, Ports and Vec

```
//Example using Asynchronous memory
import chisel3._
import chisel3.util._

class IO_Interface extends Bundle{
  // input using a Vector of 4 values
  val data_in = Input(Vec(4, (UInt(32.W))))

  val data_selector = Input(UInt(2.W)) // vector selection lines
  val data_out = Output(UInt(32.W)) // output data
  val addr = Input(UInt(5.W)) // address lines
  val wr_en = Input(Bool()) // high for write
}

class Mem_bundle_intf extends Module {
  val io = IO(new IO_Interface)
  val memory = Mem(32, UInt(32.W)) // Make memory of 32x32

  io.data_out := 0.U

  when(io.wr_en) {
    // Write at addr, with selected data from data_in vector
    memory.write(io.addr, io.data_in(io.data_selector))
  } .otherwise {
    // Asynchronous read from addr location
    io.data_out := memory.read(io.addr)
  }
}

println((new chisel3.stage.ChiselStage).emitVerilog(new Mem_bundle_intf()))
```

Flipped and Bulk Connection

```
import chisel3._
import chisel3.util._

class Interface extends Bundle {
  val in_data  = Input(UInt(6.W))
  val valid    = Output(Bool())
  val out_data = Output(UInt(6.W))
}

class MS_interface extends Bundle {
  val s2m = Input(UInt(6.W))
  val m2s = Output(UInt(6.W))
}

class Top_module extends Module {
  val io = IO(new Interface)

  val master = Module(new Master)
  val slave  = Module(new Slave)
  //connecting top with master => same direction, same name connects
  io <> master.io.top_int
  //connecting master with slave => opposite direction, same name connects
  master.io.MS <> slave.io
}
```

Flipped and Bulk Connection Cont'd

```
class Master extends Module {  
  val io = IO(new Bundle {  
    val top_int = new Interface  
    val MS = new MS_interface  
  })  
  
  io.MS.m2s := io.top_int.in_data  
  io.top_int.valid := true.B  
  io.top_int.out_data := io.MS.s2m  
}  
  
class Slave extends Module {  
  val io = IO(Flipped(new MS_interface))  
  
  io.s2m := io.m2s + 16.U  
}  
  
println(chisel3.Driver.emitVerilog(new Top_module))
```

Reading List

- Read the relevant sections from Chapters 2 and 4 of [[Schoeberl, 2019](#)]
- Also consult the [[chisel3, 2020](#)] for further details

References



chisel3 (2020).

Chisel3 library reference.

<https://www.chisel-lang.org>.



Schoeberl, M. (2019).

Digital Design with Chisel.

Kindle Direct Publishing.

